

Introduction to Energy

- **Work** is force applied over a distance. It is expressed in units such as foot-pounds (ft.-lb) or inch-pounds (in.-lb).
 - The formula for work is: **$F \times D = Work$** . In the formula, **F** is the **force** in pounds, and **D** is the **distance** in feet.
 - Example: If a 10-pound weight is lifted one foot, the work accomplished equals **10 foot-pounds**.

$$\bullet \quad 10 \text{ lb.} \times 1 \text{ ft.} = 10 \text{ ft. lb}$$

- **Power (P)** is the amount of work done based on a time period such as seconds or minutes. Power is the time rate of doing work.
 - The formula for power is:


$$\underline{\text{Power}} = \frac{\underline{\text{Work}}}{\underline{\text{Time}}}$$

- Continuing with the example from above, if a 10 pound weight was moved one foot in $\frac{1}{2}$ (.5) second, the power expended would equal **20** foot-pounds per second.

$$\underline{20 \text{ ft.-lb/second}} = \frac{\underline{10 \text{ ft.-lb}}}{\underline{.5 \text{ second}}}$$


- **Horsepower (hp)** is used for stating mechanical power. Electrical machines such as motors are rated in horsepower.
 - **One horsepower (hp)** is defined as a work rate of 550 ft.-lb/second. In addition, 33,000 ft.-lb/minute equals one horsepower.
- The unit of power is the **watt (W)**. It was named in honor of James Watt, who is credited with the invention of the steam engine.
 - The formula for electrical power is: **$P \text{ (watts)} \times E \text{ (volts)} \times I \text{ (amperes)}$** .

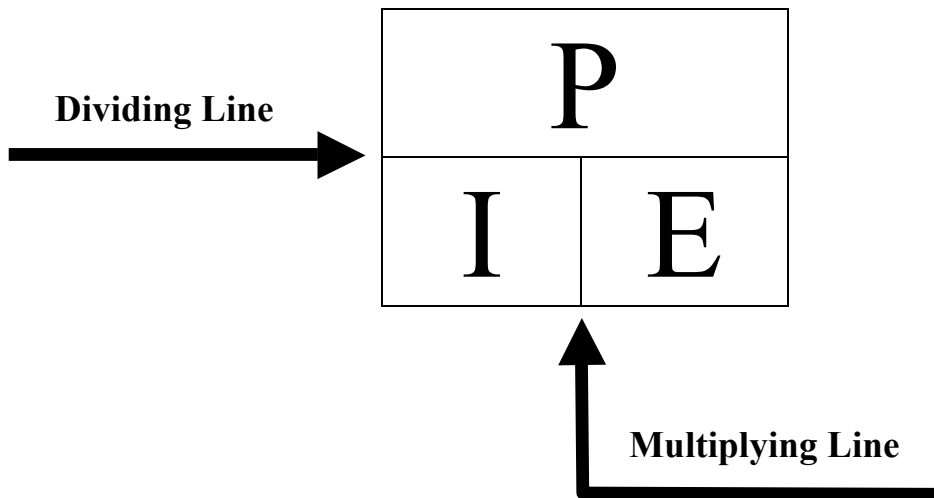- In order to convert electrical power, in watts, into mechanical power, in horsepower, you can use the following conversion factor.
 - 746 watts = 1 horsepower
- The power formula is sometimes called ***Watt's Law***, and it can be arranged algebraically. If two quantities are known, the third unknown can be found using the guide below.



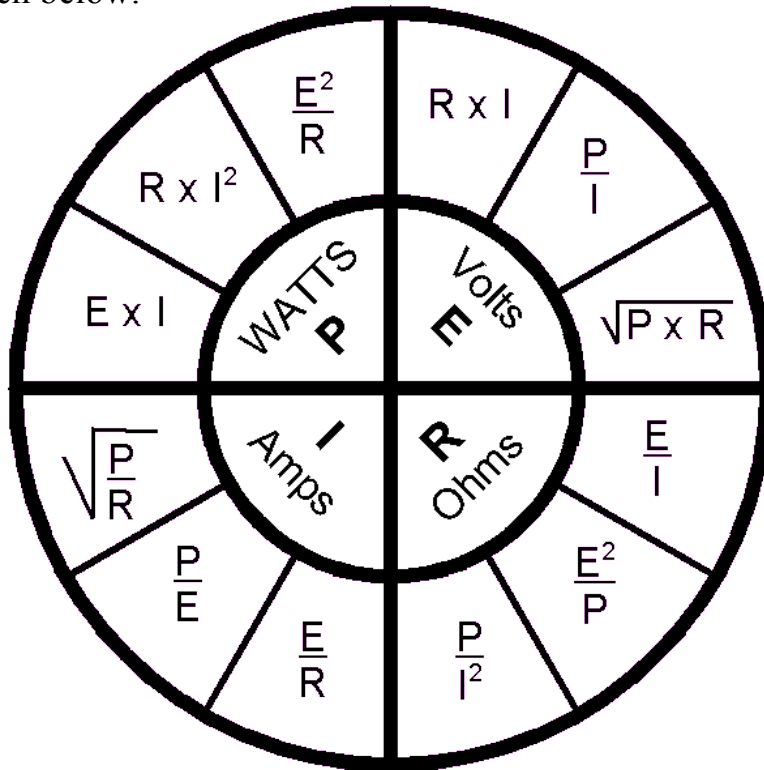- Example 1: A circuit with an unknown load has an applied voltage of 120 volts. The measured current is 8 amperes. How much power is consumed?
 - $P = I \times E$
 - $P = 8 A \times 120 V$
 - $P = 960 W$
- Example 2: A coffee pot, rated at 200 watts, is connected to a 120 volt source. How much current will this appliance use?
 - $I = P/E$
 - $I = 200 W / 120 V$
 - $I = 1.67 A$
- It is possible to combine ***Ohm's law*** and ***Watt's law*** to produce simple formulas that allow you to solve for current, voltage, resistance, or power if any two of those quantities are unknown.
 - The formulas that relate to Ohm's law and Watt's law can be arranged in a wheel-shaped guide for you to use as a reference. When you look at the guide, you will see two circles, an inner circle, and an outer circle. You will need to use the ***inner circle*** to solve for your unknown quantity. and use the ***outer circle*** to plug in your known quantities.

- The wheel shaped guide that incorporates Ohm's law and Watt's law can be seen below.



- Example 1: Using the guide above, solve the following problem. A circuit has 60 volts and a resistance of 15 ohms. How many amps and watts are involved in this circuit?

- $I = E / R$
- $I = 60 V / 15 \Omega$
- $I = 4 A$
- $P = E^2 / R$
- $P = 60^2 V / 15 \Omega$
- $P = 240 W$

- Example 2: Using the guide above, solve the following problem. A circuit has 5 amps and 50 watts. How many volts and ohms are involved in this circuit?

- $E = P / I$
- $E = 50 W / 5 A$
- $E = 10 volts$
- $R = P / I^2$
- $R = 50 W / 5^2 A$
- $R = 2 \Omega$