

Name \_\_\_\_\_


Date \_\_\_\_\_

West Islip Technology Department


Period \_\_\_\_\_
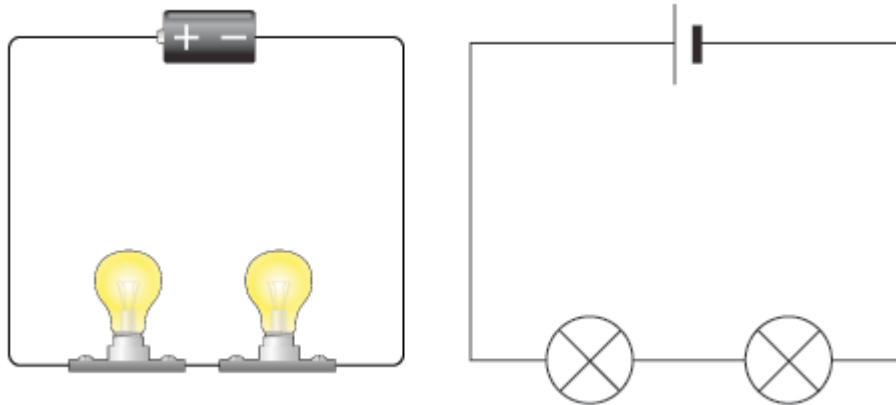
## Introduction to Series & Parallel Circuits

- \_\_\_\_\_ and \_\_\_\_\_ are two important concepts when dealing with electricity.
- There are \_\_\_\_\_ ways that a \_\_\_\_\_ can be connected in a circuit, either series or parallel.
- The circuit below has two lamps connected to a battery. In this circuit, there is only \_\_\_\_\_ over which the electrons can flow. When electrons only have one path to follow, that circuit is called a \_\_\_\_\_. The lamps are said to be wired in series with respect to each other.



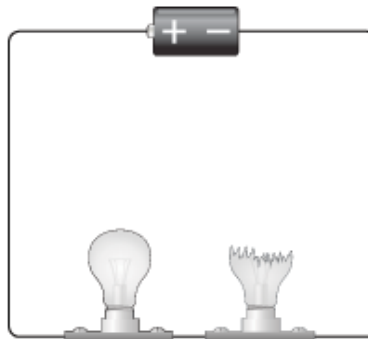
- When \_\_\_\_\_ lamps are added to a series circuit, the lights will become \_\_\_\_\_ than before.
- In a series circuit, if a lamp \_\_\_\_\_ or a component is \_\_\_\_\_, the circuit is \_\_\_\_\_ and all the components stop working. See the image below.




- Series circuits are useful if you want a \_\_\_\_\_ that one of the components in the circuit has failed. They also use \_\_\_\_\_ than parallel circuits.
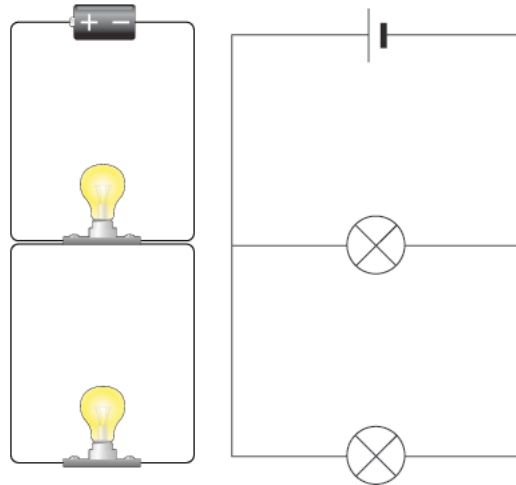
## Introduction to Series & Parallel Circuits cont...

- The circuit below has two lamps connected to a battery and they are connected in \_\_\_\_\_. In this circuit, there are \_\_\_\_\_ different paths for the electrons to follow from battery terminal to battery terminal. When electrons have more than one path to follow, that circuit is called a \_\_\_\_\_.



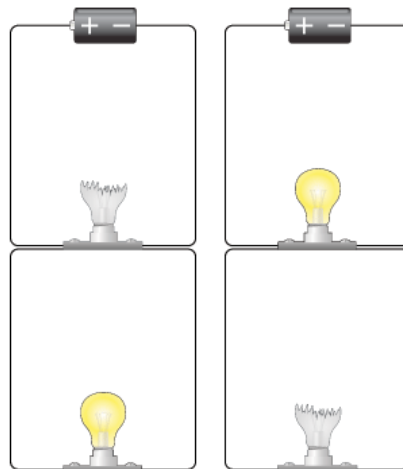- In a parallel circuit, if a lamp breaks or a component is disconnected from one \_\_\_\_\_, the components on different branches \_\_\_\_\_. And, unlike a series circuit, the lamps \_\_\_\_\_ if you add more lamps in parallel. See the image below.



- Parallel circuits are useful if you want \_\_\_\_\_, even if one component has failed. This is why our \_\_\_\_\_ are wired up with parallel circuits.