

Name _____

Date _____

West Islip Technology Department

Period _____

Introduction to Ohm's Law

- _____ is a mathematical relationship between current (I), voltage (E), and resistance (R), discovered by _____.
- Ohm's law states that the _____ measured in amperes (I) in a circuit is _____ to the applied voltage (E) _____ by the resistance (R).
- Ohm's law is expressed in three formulas below.
 - _____
 - This formula is used to determine that applied voltage is equal to the current multiplied by the resistance.
 - _____
 - This formula is used to determine that current is equal to applied voltage divided by the resistance
 - _____
 - This formula is used to determine that resistance is equal to the applied voltage divided by the current.
- Ohm's law can be applied easily by using the memory device below.

